
Name : Kemas Muhamad Kevin

Class / NIM : X / L200184134

Exercise 1

1. Make Logic Gates on picture

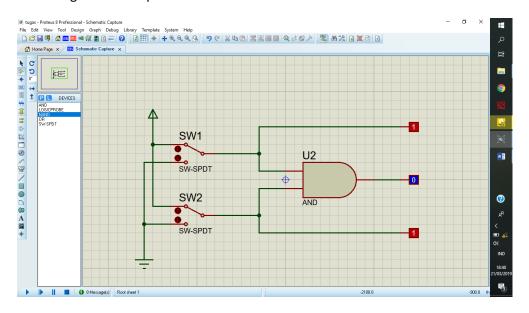


2. Truth Table.

| S W | SW | | | |
|-----|----|----|----|----|
| 1 | 2 | L1 | L2 | L3 |
| 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

| L1 | | |
|----|--|--|
| | | |
| L2 | | |
| LZ | | |
| L3 | | |
| | | |

1. Make Logic Gates on this picture

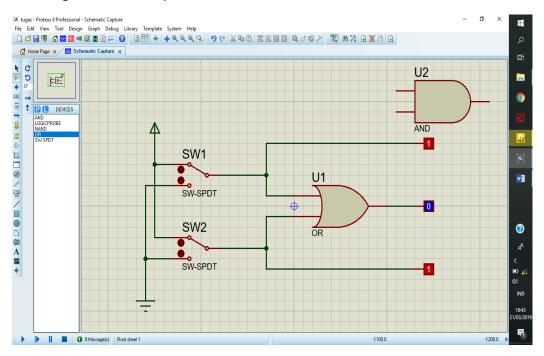


2. Truth Table.

| S W | SW | | | |
|-----|----|----|----|----|
| 1 | 2 | L1 | L2 | L3 |
| 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 1 | 1 |




1. Make Logic Gates on this Picture.

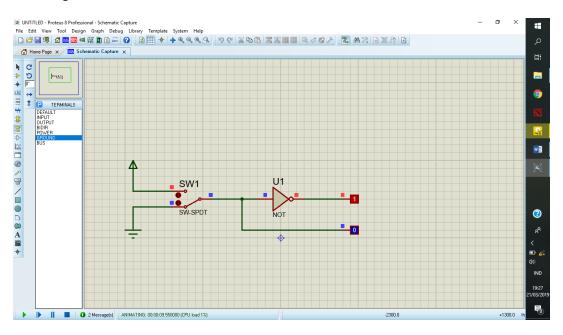


2. Truth Table.

| S W | | |
|-----|----|----|
| 1 | L2 | L1 |
| 0 | 0 | 1 |
| 1 | 1 | 0 |

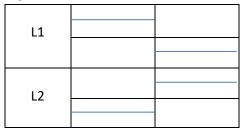

1. Make Logic Gates on this Picture.

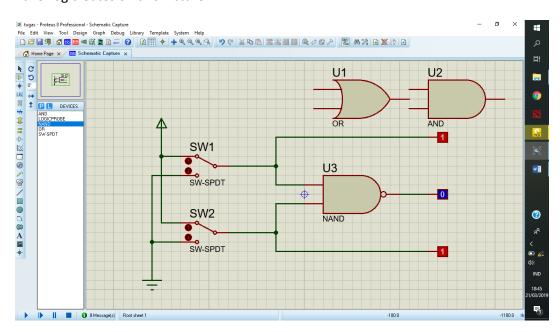


2. Truth Table.

| S W | SW | | | |
|-----|----|----|----|----|
| 1 | 2 | L1 | L2 | L3 |
| 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 1 | 0 |



1. Make Logic Gates on this Picture.

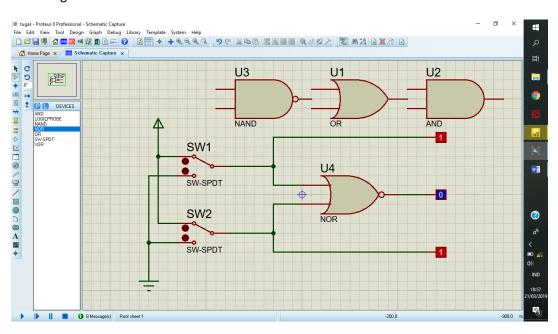


2. Truth Table.

| S W | SW | | | |
|-----|----|----|----|----|
| 1 | 2 | L1 | L2 | L3 |
| 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 0 |



1. Make Logic Gates on this Picture.

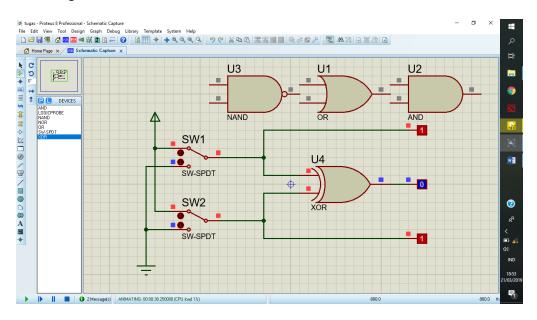


2. Truth Table.

| S W | SW | | | |
|-----|----|----|----|----|
| 1 | 2 | L1 | L2 | L3 |
| 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 1 | 0 |



1. Make Logic Gates on this Picture.

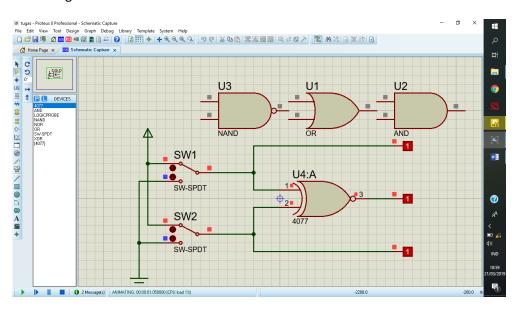

2. Truth Table.

| S W | SW | | | |
|-----|----|----|----|----|
| 1 | 2 | L1 | L2 | L3 |
| 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

| L1 | | |
|----|---|--|
| | | |
| | | |
| | | |
| L2 | | |
| | | |
| | | |
| | , | |
| L3 | | |
| | | |
| | | |